

Hkkjrh; izkS|ksfxdh LkaLFkku iVuk

Indian Institute of Technology Patna

Department of Electrical Engineering

IIT Patna, Campus, Bihta, Patna, Bihar – 801103

Experiment- 7

VOLTAGE TO FREQUENCY CONVERTER

OBJECTIVE: Designing a voltage to frequency converter.

MATERIALS REQUIRED

Components :

Op-Amp : Two LM741.
Transistor : One 2N2222A
Diode : one 6.2V zener diode.
Resistance : One 330, One 1k Ω , two 2.2K Ω , one 3.9K Ω , one 5.6K Ω , two 10 k Ω , three 100 k Ω .
: Capacitor : One 10 μ F.

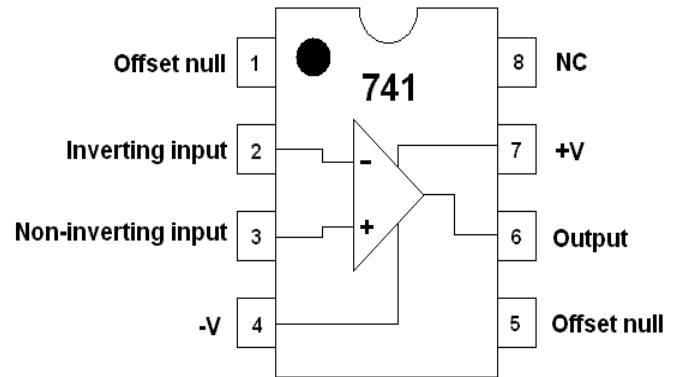


Fig 7.1

PRECAUTIONS AND GUIDELINES

1. The op-amp (Fig 7.1) generally works on split power supply (e.g. ± 12 V). Both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from ± 5 V to ± 15 V. Do not forget to connect the common terminal of the power supply to the *ground* on the breadboard.
2. Connecting only one side of power supply or interchanging positive and negative power supplies damages the op-amp.
3. While switching on the set-up, switch on the oscilloscope first, then the power supply to the circuit, and finally the function generator. When switching off, follow the sequence in reverse order.
4. For any IC, never exceed the input voltage beyond the power supply limits.
5. Keep ground terminals of the oscilloscope probes and function generator output, and power supply common connected together throughout the experiment.

The circuit shown in Fig. 7.2 is of Voltage to Frequency converter

Working Principle: Initially, the capacitor C gets charged at constant rate of (V_i / R_3) amp. The output voltage V_a at point 'a' drops linearly till this voltage is not less than the voltage V_b at point 'b' which is approx. at about -5.0V. Note that, the comparator output voltage V_C is at approx. -12V when V_a is greater than -5.0V and the transistor is in 'off' state.

When the negatively increasing voltage V_a becomes less than -5.0V, the comparator output V_c goes to approx. +12V. The transistor gets 'on' and hence the emitter voltage (also voltage at comparator '+' input) of the transistor is about at zero voltage. The transistor is in saturated state. The capacitor starts discharging. The discharging continues and V_a increases positively, till V_a becomes greater than zero voltage. The comparator output V_C becomes about -12V and the transistor becomes 'off'. This charging and discharging process repeats again and again. Note that the discharging duration is same for any input voltage V_i and it should be much smaller than the charging time, which depends on the input voltage V_i .

Pre-experiment Reading:

- (a) Draw the waveforms at (i) V_a (ii) V_b and (iii) V_c
- (b) Compute the charging time of the capacitor.
- (c) Compute the discharging time of the capacitor.
(Assume $V_i = 4V$ for above)

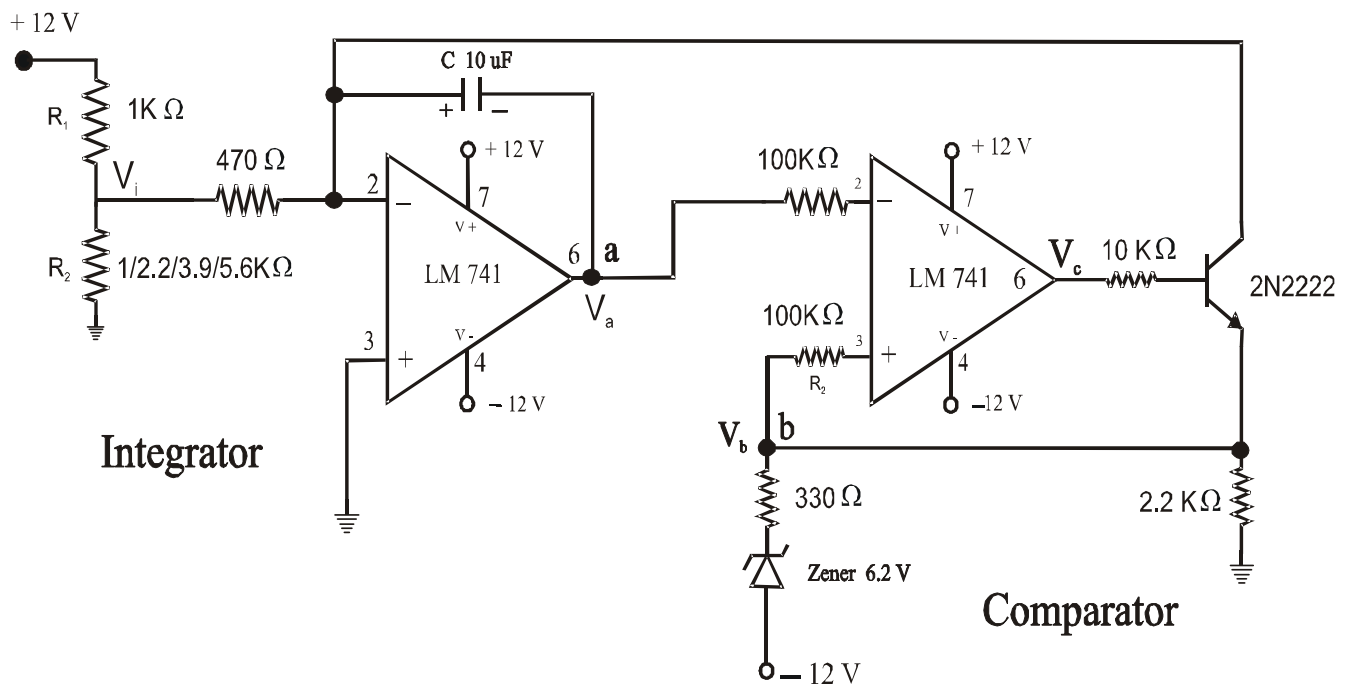


Fig 7.2 Voltage to Frequency Converter

OBSERVATIONS:

1. Connect the circuit as shown in Fig 7.2 with $R_1 = 1\text{ k}\Omega$, and $R_2 = 1\text{ k}\Omega$. Make sure the power supply ground is connected to the circuit ground.
2. Observe the waveform V_a at point 'a' for
 - (a) for $R_2 = 1\text{ k}\Omega$
 - (b) for $R_2 = 2.2\text{ k}\Omega$
 - (c) for $R_2 = 3.9\text{ k}\Omega$
 - (d) for $R_2 = 5.6\text{ k}\Omega$and measure frequency from the output at point (V_c)
3. Similarly, observe the waveform V_b at point 'b' for all V_i as in step 2.
4. Remove the zener diode and replace it by a resistance so that V_b is approx. at $-5.0V$ and observe V_b (both frequency and pulse width).
