

# Hkkjrh; izkS|ksfxdh LkaLFkku iVuk

Indian Institute of Technology Patna

Department of Electrical Engineering

IIT Patna, Campus, Bihta, Patna, Bihar – 801103

Experiment No:-2

## DIODE CIRCUITS

**OBJECTIVES:** Design and analysis of half wave rectifier and clipping circuits.

### MATERIALS REQUIRED


- Components :**  
Diode : One: Type 1N4007  
Zener Diode : One: (voltage  $V_Z = 3.3\text{ V}$ )  
Resistance : Five:  $470\ \Omega$ ,  $56\ \Omega$ ,  $1\text{ K}\Omega$ ,  $2.2\text{ K}\Omega$ ,  $4.7\text{ K}\Omega$   
Capacitor : One:  $22\ \mu\text{F} 25\text{V}$ .

### GENERAL GUIDELINES / PRECAUTIONS


- Connect the capacitor with correct polarity. The capacitor being of electrolytic type, it is polarized, and will be damaged if connected with incorrect polarity. Similarly, confirm the polarity of the diodes before connecting.
- Keep ground terminals of oscilloscope probes and function generator output connected together throughout the experiment.
- In an oscilloscope, for higher precision, increase vertical sensitivity (i.e. lower value of volt/div), especially while measuring small amplitude levels (e.g. ripple voltage). You may need to switch to ac coupling while doing so.
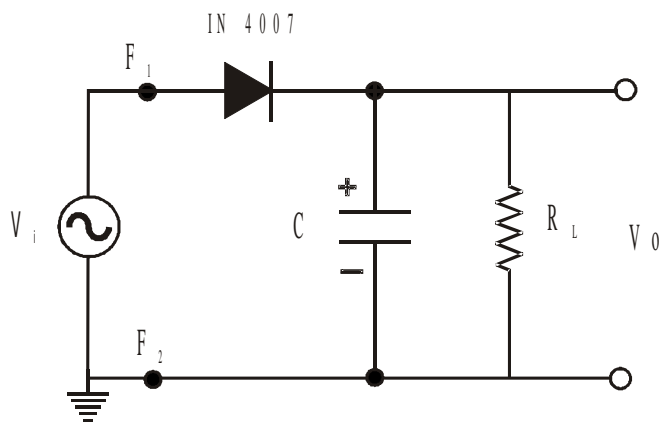
### PART A : HALF - WAVE RECTIFIER WITHOUT FILTER

- Set the function generator to get 10 V peak-to-peak sine wave (in High Z load mode) at 500 Hz frequency. Do not connect any circuit to the function generator. Keep dc offset equal to 0. Observe the function generator output on the oscilloscope and verify sine wave generation.
- Set up the circuit as shown in Fig. 2.1(a) without the capacitor C, taking  $R_L = 2.2\text{ k}\Omega$ .
- Now, connect the function generator to the circuit at points F1 & F2 as shown in Fig. 2.1(a).
- Display  $V_i$  and  $V_o$  simultaneously on the oscilloscope. **Sketch**  $V_i$  and  $V_o$  one below the other with identical time and amplitude axes.



(a)

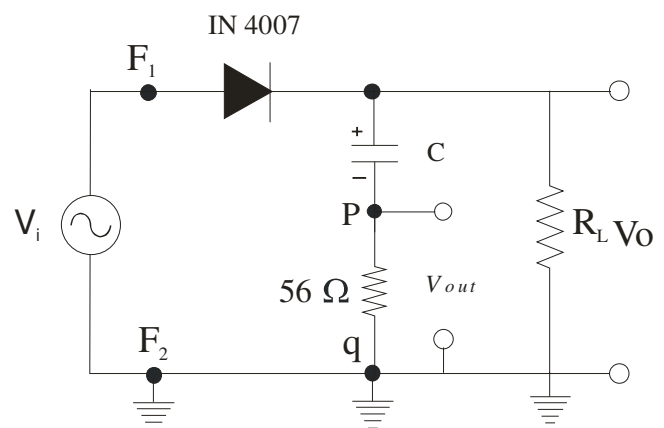

(b)

Fig. 2.1 Half-wave rectifier

### PART B: HALF - WAVE RECTIFIER WITH CAPACITOR FILTER

1. Now connect a capacitor  $C = 22 \mu\text{F}$  in the circuit with correct polarity as shown in Fig. 2.1(a).
2. Display  $V_i$  and  $V_o$  simultaneously on the oscilloscope. **Sketch**  $V_i$  and  $V_o$  overlapping, with the same time and amplitude axes.
3. **Measure** peak-to-peak ripple voltage on oscilloscope by enlarging  $V_o$  to the maximum extent. You may have to put the input coupling in ac mode while doing this measurement. See the guidelines given at the end.

Repeat steps 2 and 3 for  $R_L = 2.2\text{K}\Omega$  and  $4.7 \text{ K}\Omega$ . **Comment** on the output waveforms and ripple voltages.

4. Connect a  $56\Omega$  resistance in series with  $C$  of Fig. 2.1(a) as shown in Fig. 2.1(b). The points across this  $56\Omega$  resistor are marked as **p** and **q**.

**Please note that:** The resistance  $56\Omega$  is chosen small enough not to affect the overall performance of the circuit and at the same time to ensure an appreciable voltage across it. This voltage represents the current flowing through the capacitor.

5. Display and **sketch**  $V_o$  and  $V_{56}$  (i.e. voltage across  $56\Omega$  between 'p' and 'q') one below the other with identical time axes. Mark the ground reference line.

**Q. 1:** Why is  $I_C (=V_{470} \Omega / 470 \Omega)$ , the current through the capacitor, negative for some portion of a cycle? Estimate  $I_{\text{surge}}$  (positive peak of  $I_C$ ).

### PART C : CLIPPING CIRCUIT - POSITIVE CLIPPER

1. Connect the circuit as shown in Fig. 2.2 with  $R = 2.2 \text{ K}\Omega$
2. Set the function generator to get 10 V peak-to-peak sine wave (in High Z load mode) at 500 Hz frequency. Observe the function generator output on the oscilloscope and verify sine wave generation.
3. Connect the function generator output to the circuit as shown in Fig. 2.2.
4. Display and **sketch**  $V_i$  and  $V_o$  one below the other with identical time and amplitude axes.
5. Superimpose the two waveforms  $V_i$  and  $V_o$  and observe
6. Set the oscilloscope in X-Y mode ( $V_i$  to Ch2 : X-input and  $V_o$  to Ch1 : Y-input) and **sketch**  $V_o$  versus  $V_i$  with equal x and y scales. Label the graph and ticks on the axes.

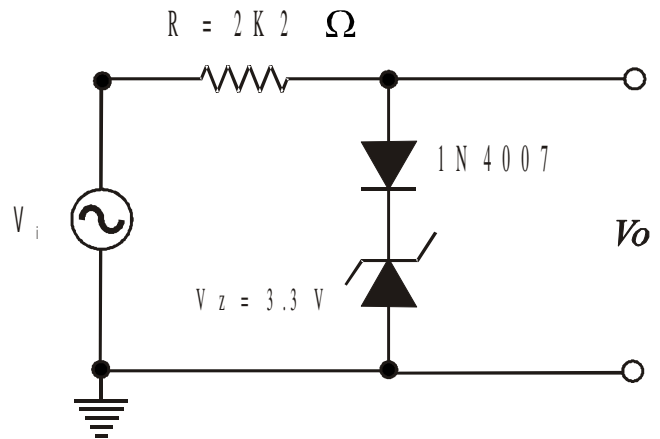


Fig. 2.2 Positive clipper

**Q. 2:** Draw the circuit diagrams for: (a) -ve clipper (b) +ve and -ve clipper

#### Pre observation reading:

(a) Draw the expected waveforms at –

(i) Step no. 4 of PART A, (ii) Step no. 2 of PART B and (iii) Step no. 4 of PART C.

**Q.3:** Why electrolytic capacitor has polarity.

