



Study of Common-Emitter Amplifier

OBJECTIVES:

1. To carry out an approximate DC and AC-analysis of the given CE amplifier.
2. To determine the voltage gain, the “maximum undistorted peak-to-peak output voltage swing” (MUOVS) and the maximum input voltage for undistorted output.
3. To study the effects of emitter bypass capacitor on voltage gain.

MATERIALS REQUIRED

1. Breadboard : One
- Transistor : One- NPN type 2N2222A.
- Resistor : Five - 470 Ω , 1K, 2.2 K, 22 K, 100K.
- Capacitor : Three - 10 μ F, 10 μ F, 22 μ F

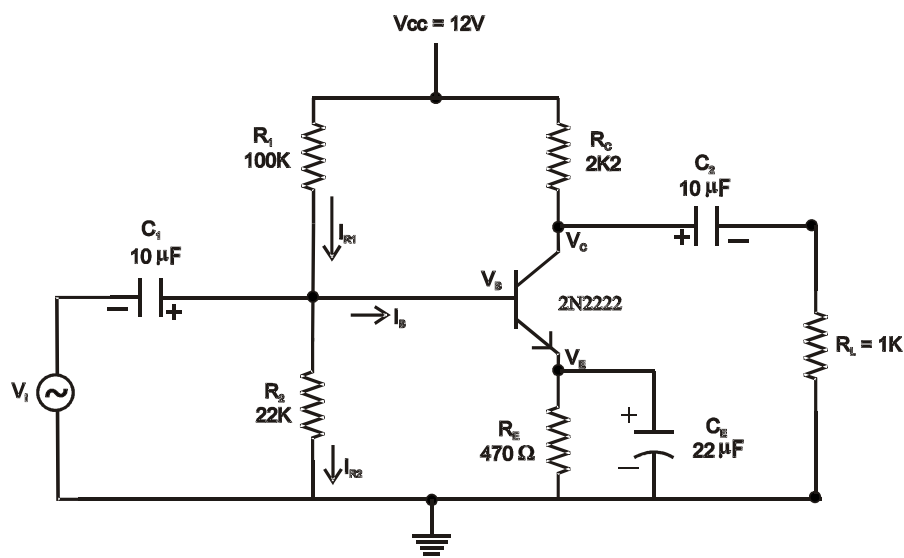


Fig. 1: Common-emitter amplifier

Important: You are expected to complete Part 1 at home and come to the Lab with a neat report showing all calculations. You will be allowed to continue with the rest of the experiment only after the instructor has checked the report.

Part-I. Pre-experiment preparation

Approximate DC and AC-analysis:

Carry out an approximate DC-analysis by using the values given in Fig. 1 and by making use of the following assumptions:

(a) $I_{R1}, I_{R2} \gg I_B$, so that $I_{R1} \approx I_{R2}$

(b) $V_{BE} \approx 0.65$ V

Under these assumptions, you should be able to estimate the

(C) DC quantities (quiescent values) $V_B, V_E, V_C, I_C (\approx I_E)$

$$\text{Voltage Gain } A_v = \frac{-\beta R_C}{r_b} = -\frac{R_C}{r_b/\beta} \approx -\frac{R_C}{r_e} = -\frac{R_C}{V_T/I_E}$$

$$= -\frac{R_C I_E}{V_T} \approx -\frac{\beta R_C I_C}{V_T} \quad (4.1)$$

Where $V_T = \frac{kT}{q}$: the thermal voltage; k = Boltzmann's constant = 1.38×10^{-23} J/K

$q = 1.6 \times 10^{-19}$ Coulomb, T is temperature in Kelvin.

Take $V_T \approx 25\text{mV}$ at a room temp of 20°C)

In (4.1), we have used the approximation $r_b = (\beta + 1)r_e \approx \beta r_e$

Note: The approximation does not require the knowledge of β

$$\text{MUOVS} = 2 * \text{Min} \{ V_{CC} - V_C, V_C - V_E \}$$

Q: (connecting an electrolytic capacitor) How do you decide that the + ve terminal of C_1 should be connected to the $R_1 - R_2$ node and the -ve terminal to the source V_i ? Likewise, for C_2 and C_E .

2.1 Experimental determination of the quiescent voltages and currents:

(a) Before assembling the circuit, measure the actual values of the resistors by means of a Digital Multi Meter (DMM).

[Remember you are using resistors with 10% tolerance]. The actual values are to be used in determining the currents.

(b) Now assemble the circuit, apply V_{CC} and note the following:

- measure V_{BE} using DMM; it should be around $0.6 \sim 0.7$ V indicating that B_E -junction is forward biased.
- Measure V_C and check if $V_E < V_C < V_{CC}$. A value of V_C midway between V_E and V_{CC} is preferable (Q1: Why is such a value preferable?).

If your measurements agree, you are along the right path.

(c) Now measure V_B , V_E , V_C and V_{CC} ; then using the measured resistance values, determine I_B , I_E , I_C and hence β ($\beta = I_C / I_B$).

(d) Compare the experimentally determined values of the currents and voltages with those you obtained through approximate analysis.

(e) Compare the experimentally determined value of β with the approximate value stated in the manual or given by the Lab Instructor.

(f) Compute A_v (equation 4.1) using the experimentally determined values of R_C and I_C . Use $V_T = 25\text{mV}$.

2.2 Voltage gain without load resistance R_L :

Disconnect C2.

Adjust FG to get approximately 20mV peak-to-peak sinusoid at 1 kHz (display in Ch- 1). Apply this voltage at amplifier input (V_i).

Display collector voltage in Ch-2 of DSO (use DC-coupling). Note the 180° phase difference between the input and the output. Adjust V_i amplitude to get a convenient value for peak-to-peak collector voltage V_C, PP (say 3.6 V).

Note the corresponding V_i, PP (mV). Experimentally obtained voltage gain is therefore:

$$A_v = \frac{-V_C, PP}{V_i, PP}$$

Compare this value with the computed values obtained in step 2.1(f). Also compare this value with the value estimated in your pre-reading assignment.

3. Maximum undistorted output voltage swing (MUOVS)

Increase V_i slowly till you observe a slight flattening of V_C waveform at its peaks (either positive peaks or negative peaks). The peak-to-peak value of the output signal (just at the onset of distortion/clipping) is the MUOVS. Measure the corresponding V_i , PP, the peak- to-peak input voltage.

This information is useful in an amplifier: it tells the user that the input should not exceed this value for faithful amplification of the signal, else distortions sets in.

Now increase V_i beyond this point and observe the output waveform. The sinusoid gets increasingly flattened and becomes more like a square wave. (Overdriving an amplifier leads to heavy distortion)

[!! Square-wave from a sine-wave]

4. Voltage-gain with load resistance R_L :

The output of an amplifier normally drives a load resistance R_L which may represent an actual load like an ear-phone or a loudspeaker, or the input impedance of another state of amplifier.

Connect R_L (see circuit) to the collector through the coupling capacitor C_2 (C_2 blocks the DC voltage at the collector and allows only the AC i.e. the signal component to pass through).

Measure A_V with R_L connected. (You would observe a reduced A_V since $R_{C, eff} = R_C || R_L$).

5. Effect of C_E on A_V :

Get back to the conditions in Part 2.2 i.e. V_i at 1 KHz, its amplitude adjusted to get V_C , PP 3.6V approx. Now, remove C_E (with ckt. powered) and note the drastic reduction in V_C , PP. You have to change to appropriate V/div in your DSO. Determine the gain of the C_E amplifier with unbypassed R_E

Compare your observation with the theoretical value

$$A_V = - \frac{\alpha R_C}{R_E + r_e} \approx - \frac{R_C}{R_E} \quad (4.2)$$

- Display and sketch V_i and V_E waveforms. Note the amplitudes and the phase-relationship between them.
- Display and sketch V_E and V_C . Note the amplitudes and the phase relationship. Please note that you are in DC coupling mode of the DSO. Please ensure that when you pressed the ground options in CH1 and CH2, both the horizontal traces (of CH1 and CH2) are coinciding. Also ensure that the V/div of CH1 is equal to V/div of CH2.
- Increase V_i gradually and observe how V_E and V_C change. Continue to increase V_i till you observe the +ve peak of V_E (almost) touching the negative peak of V_C . When this occurs, we say that the BJT has gone into saturation ($V_{CE} \approx 0$).

Q2: What do you observe if V_i is increased beyond this point?