

# Hkkjrh; izkS|ksfxdh LkaLFkku iVuk

Indian Institute of Technology Patna

Department of Electrical Engineering

IIT Patna, Campus, Bihta, Patna, Bihar – 801103

Experiment: 5

## OPERATIONAL AMPLIFIER

**OBJECTIVE :** Realization of amplifier circuits with Op-Amp (Operational Amplifier)

### MATERIALS REQUIRED

- Components  
Op-Amp : One: LM741.  
Resistance : Five: 1 k $\Omega$  (1 no), 10 k $\Omega$  (1 no), 12 k $\Omega$  (2)




### PRECAUTIONS AND GUIDELINES

- The op-amp generally works on split power supply (e.g.  $\pm 12$  V). Both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from  $\pm 5$  V to  $\pm 15$  V. Do not forget to connect the common terminal of the power supply to the ground on the breadboard.
- Connecting only one side of power supply or interchanging positive and negative power supplies damages the op-amp.
- For connecting power supply, you have to follow the procedure as given below.
  - Disconnect the power supply to op-amps.
  - Switch on the power supply.
  - Set the output voltage as required (e.g.  $\pm 12$  V).
  - Switch off the power supply.
  - Connect the power supply to op-amps.
  - Switch on the power supply.
- For any IC, never exceed the input voltage beyond the power supply limits.
- Use the horizontal strips of the breadboard for power supply. Tap the power supply for each IC from these supply lines.
- Keep ground terminals of the oscilloscope, probes and function generator output, and power supply common connected together throughout the experiment.
- Use AFG in “High Z” mode.

### Pre-experiment Reading:

Obtain the theoretical values of  $V_o / V_i$  for step 5 of Part A. Do this for Part B also.

### PART A : INVERTING AMPLIFIER

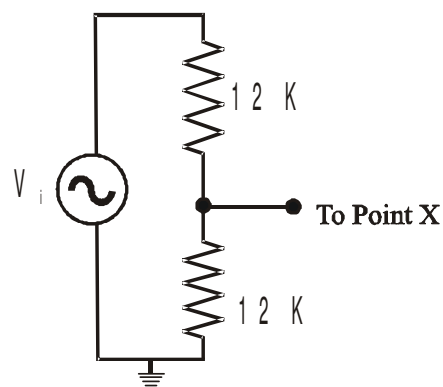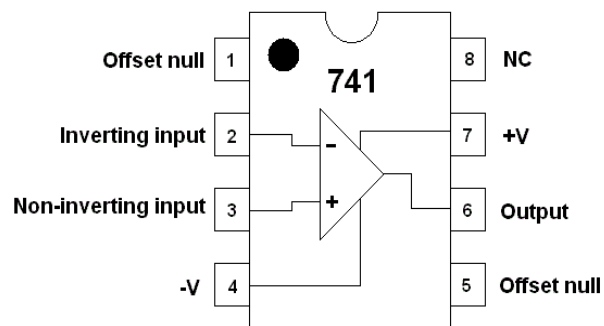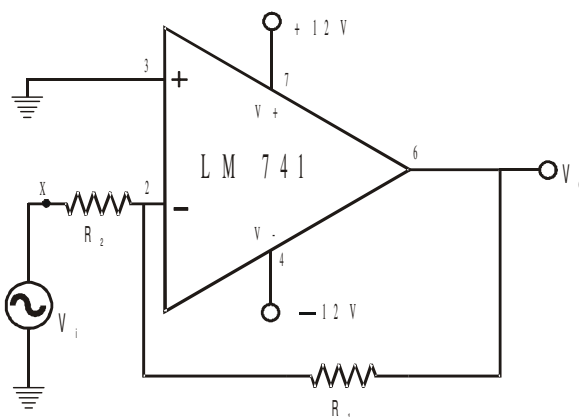

**Fig. 5.1 Inverting Amplifier****Fig 5.2 Voltage Divider**

1. Assemble the circuit shown in Fig. 5.1 with  $R_1 = 10\text{ k}\Omega$  and  $R_2 = 1\text{ k}\Omega$ . Make sure the power supply ground is connected to the circuit ground.
2. Apply 200 mVp-p, 1 kHz sine wave at  $V_i$  from the function generator and see the output.
3. Observe  $V_o$  and  $V_i$  and determine voltage gain  $A = V_o / V_i$ . Also obtain  $A$  for  $V_i = 100\text{ mVp-p}$  and  $300\text{ mVp-p}$ .
4. Change  $R_1$  &  $R_2$  to  $100\text{ k}\Omega$  &  $10\text{ k}\Omega$  respectively and determine  $A$  for  $V_i = 100\text{ mVp-p}$ ,  $200\text{ mVp-p}$  and  $300\text{ mVp-p}$ .
5. Now apply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{ mVp-p}$ ) to the point 'X' through the potential divider circuit (instead of directly connecting the source at 'X') as shown in Fig. 5.2 and note the values of  $V_o$  for


$$(i) \quad \frac{R_1}{R_2} = \frac{100\text{K}\Omega}{10\text{K}\Omega} \text{ and}$$

$$(ii) \quad \frac{R_1}{R_2} = \frac{10\text{K}\Omega}{1\text{K}\Omega}$$

Compute  $V_o / V_i$  for (i) and (ii).

#### PART B : NON-INVERTING AMPLIFIER

- 1) Assemble the circuit shown in Fig. 5.3 with  $R_1 = 10\text{ k}\Omega$  and  $R_2 = 1\text{ k}\Omega$ . Make sure the power supply ground is connected to the circuit ground.
- 2) Apply 200 mVp-p, 1 kHz sine wave at  $V_i$  from the function generator and see the output.
- 3) Observe  $V_o$  and  $V_i$  and determine voltage gain  $A = V_o / V_i$ . Also obtain  $A$  for  $V_i = 100\text{ mVp-p}$  and  $300\text{ mVp-p}$ .
- 4) Change  $R_1$  &  $R_2$  to  $100\text{ k}\Omega$  &  $10\text{ k}\Omega$  respectively and determine  $A$  for  $V_i = 100\text{ mVp-p}$ ,  $200\text{ mVp-p}$  and  $300\text{ mVp-p}$ .
- 5) Now apply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{ mVp-p}$ ) to the point 'X' through the potential divider circuit as shown in Fig. 5.2 and note the values of  $V_o$  for

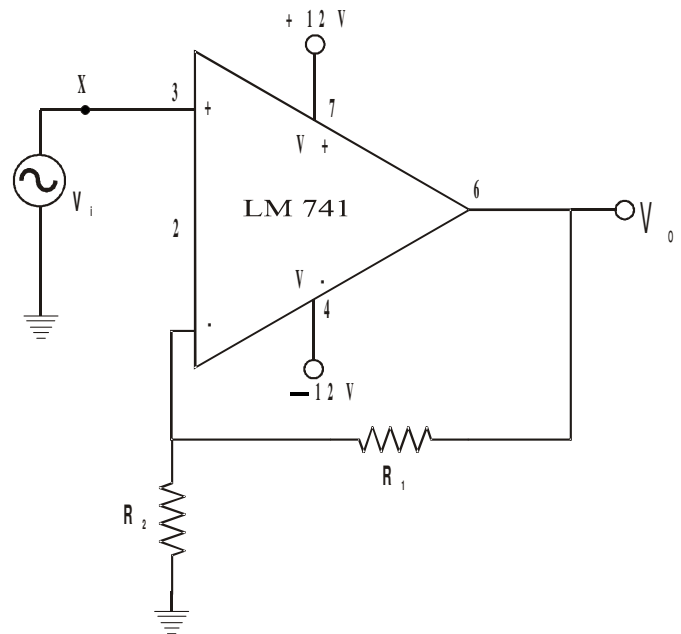
**Fig. 5.3 Non-inverting amplifier**

$$(i) \quad \frac{R_1}{R_2} = \frac{100\text{K}\Omega}{10\text{K}\Omega} \text{ and}$$

$$(ii) \quad \frac{R_1}{R_2} = \frac{10\text{K}\Omega}{1\text{K}\Omega}$$

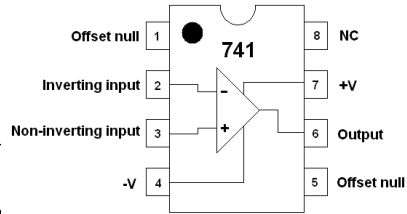
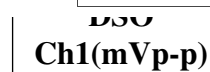

**Q1.** For a source with high internal impedance which configuration (inverting or non-inverting) will be suitable for designing a good amplifier?

**Q2.** Design an Amplifier system to obtain a gain of '-50' for a source with high internal resistance. You may use combinations of inverting and non-inverting configurations. (Make use of answer of Q1.)



## Operational Amplifier-I

Exp.-5

Sl. No.	R1	R2	<div>  </div> A <sub>VG</sub> (mVp-p)	<div>  </div> Ch1(mVp-p)	<div>  </div> Ch2(mVp-p)	Voltage Gain ( $A=V_o/V_i$ )
<b>Part A : INVERTING AMPLIFIER</b>						
1	10K	1K	100			
2	10K	1K	200			
3	10K	1K	300			
1	100K	10K	100			
2	100K	10K	200			
3	100K	10K	300			
<b>Vin Measure at Point 'X' (For Voltage Divider)</b>						
1	100K	10K	200			
2	10K	1K	200			
<b>Part B : NON-INVERTING AMPLIFIER</b>						
1	10K	1K	100			
2	10K	1K	200			
3	10K	1K	300			
1	100K	10K	100			
2	100K	10K	200			
3	100K	10K	300			
<b>Vin Measure at Point 'X' (For Voltage Divider)</b>						

1	100K	10K	200			
2	10K	1K	200			